

1/12/2010  
60min



11/15

م. محمود الدرد


الشعبة : اربعاء 5-2

الاسم : معاذ سلام قعدان

الدرجة  
11  
15

Q1) The v-I characteristics of a linear resistor is shown below . find R

i{mA}

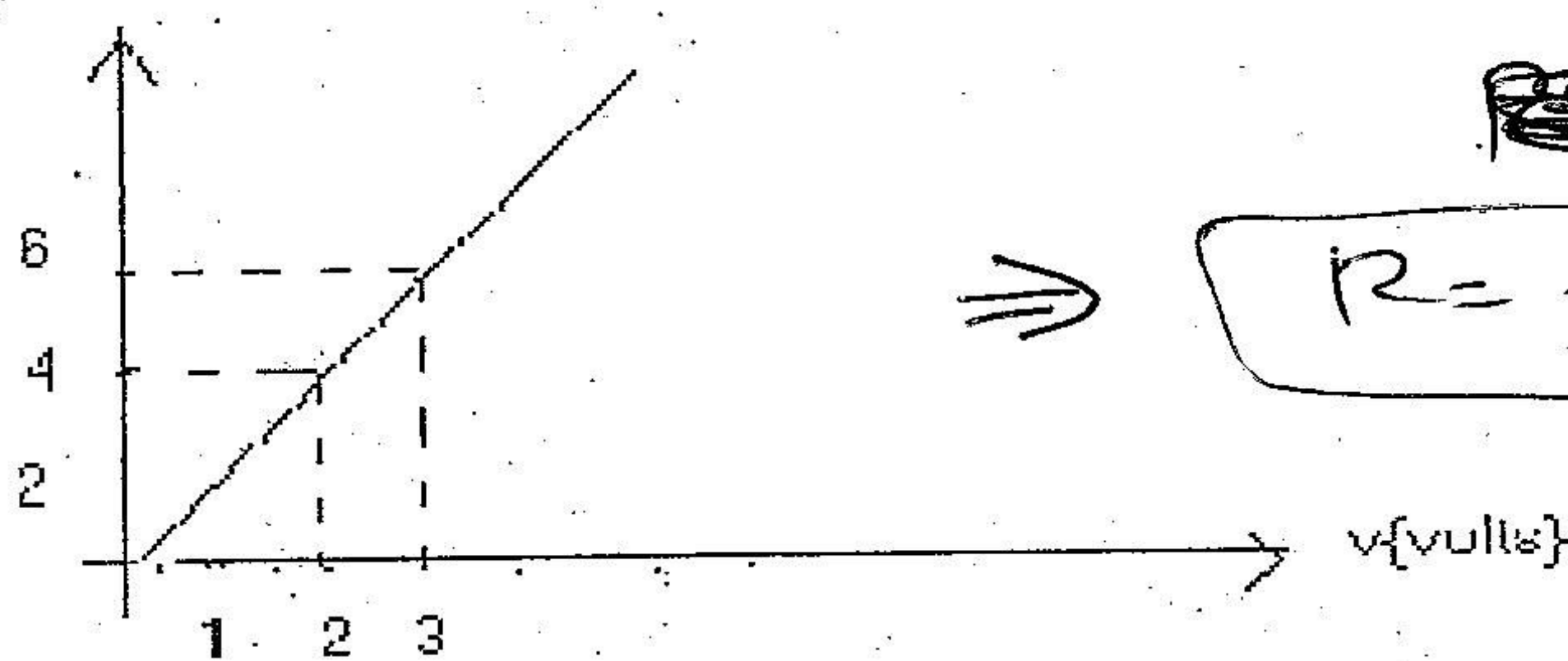


$$\Rightarrow R = \frac{1}{\text{Slope}} \Rightarrow \text{Slope} = \frac{6-4}{3-2} = \frac{2}{1} = 2$$

$$R = \frac{1}{2} \times 10^3 = \frac{1000}{2} = 500 \Omega$$

$$\therefore R = \frac{3}{6 \times 10^{-3}} = \frac{1}{2} \times 10^3 = 500 \Omega$$

$$R = 500 \Omega$$

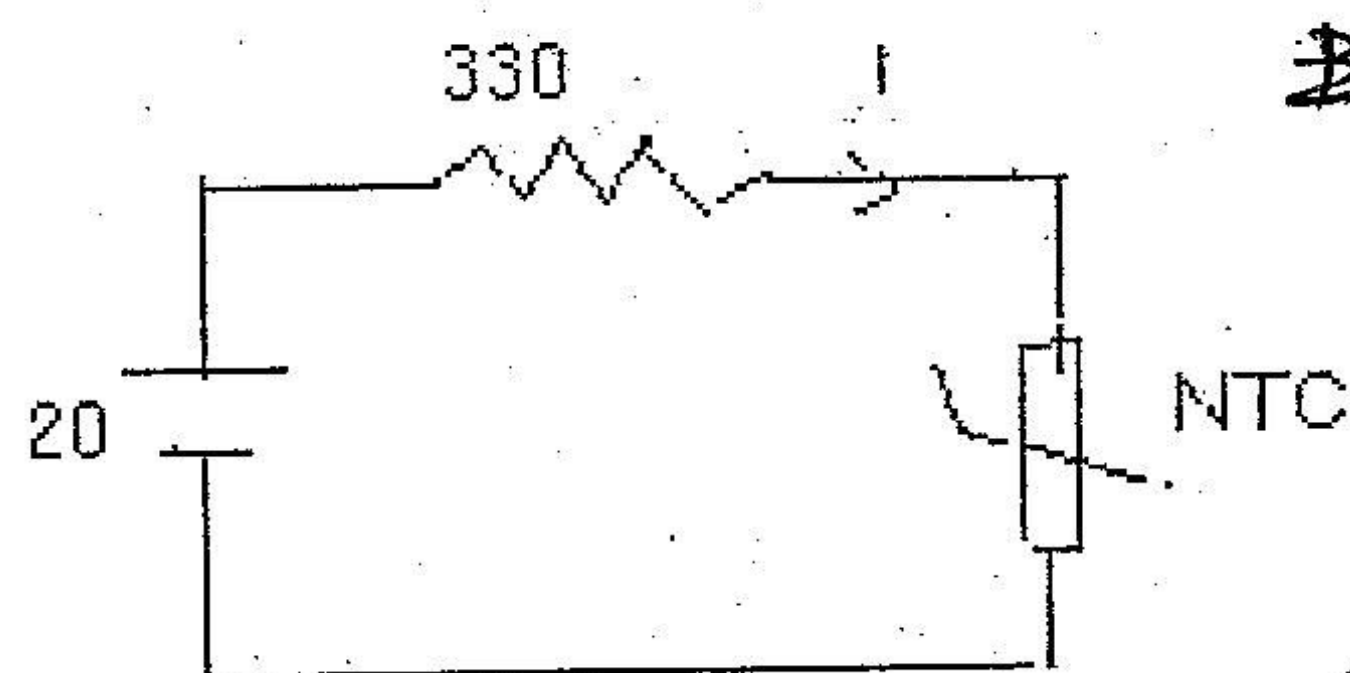Q2) In the circuit shown below the NTC is connected in series with 330Ω resistor .If the current flow stabilizes at 4m A .Find the value of the resistance of the NTC  $R_{NTC}$  & the total resistance of the circuit ( $R_{TOT}$ )



$$V = I R_{eq}$$

$$R_{eq} = 330 + R_{NTC}$$

$$R_{TOT} = 5k\Omega$$

$$R_{NTC} = 4.67k\Omega$$

$$20 = 4 \times 10^{-3} (330 + R_{NTC})$$

$$\Rightarrow 330 + R_{NTC} = \frac{20}{4 \times 10^{-3}} = 5 \times 10^3 = 5000 \Omega$$

$$\therefore R_{NTC} + 330 = 5000$$

$$\Rightarrow R_{NTC} = 5000 - 330$$

$$\Rightarrow R_{TOT} = 330 + 4670 = 5000 = 5k\Omega$$

$$= 4.67k\Omega$$

Q3) At ambient temperature of 18 c° the parallel circuit of PTC and  $R_1$  Loads the voltage source with a total resistance of 5KΩ. What is the value of PTC resistor at this temperature

$$R_{PTC} = 10k\Omega$$

$$\therefore R_{eq} = 5k\Omega$$

$$\therefore R_1 \parallel R_{PTC} = 5k\Omega$$

$$\frac{R_1 R_{PTC}}{R_1 + R_{PTC}} = 5k\Omega$$

$$\frac{10 R_{PTC}}{10 + R_{PTC}} = 5 \Rightarrow 5(10 + R_{PTC}) = 10 R_{PTC}$$

$$50 + 5 R_{PTC} = 10 R_{PTC} \Rightarrow$$

$$50 = 5 R_{PTC} \Rightarrow R_{PTC} = \frac{50}{5} = 10k\Omega$$




Q4) In the circuit shown below the LDR is connected in parallel with  $1k\Omega$  resistor. When the light beam is maximum it was found the total current in the circuit  $I_{tot} = 37 \text{ mA}$ . In dark it was found that the LDR is open circuit. Find the minimum value of the LDR resistance  $R_{LDRM}$  & the maximum & minimum voltage across the LDR.

$$V_{min} = V_s \frac{1}{1+1} = 20 \left( \frac{1}{2} \right) = 10 \text{ V}$$

$$V_{max} = V_s (1) = 20 (1) = 20 \text{ V}$$

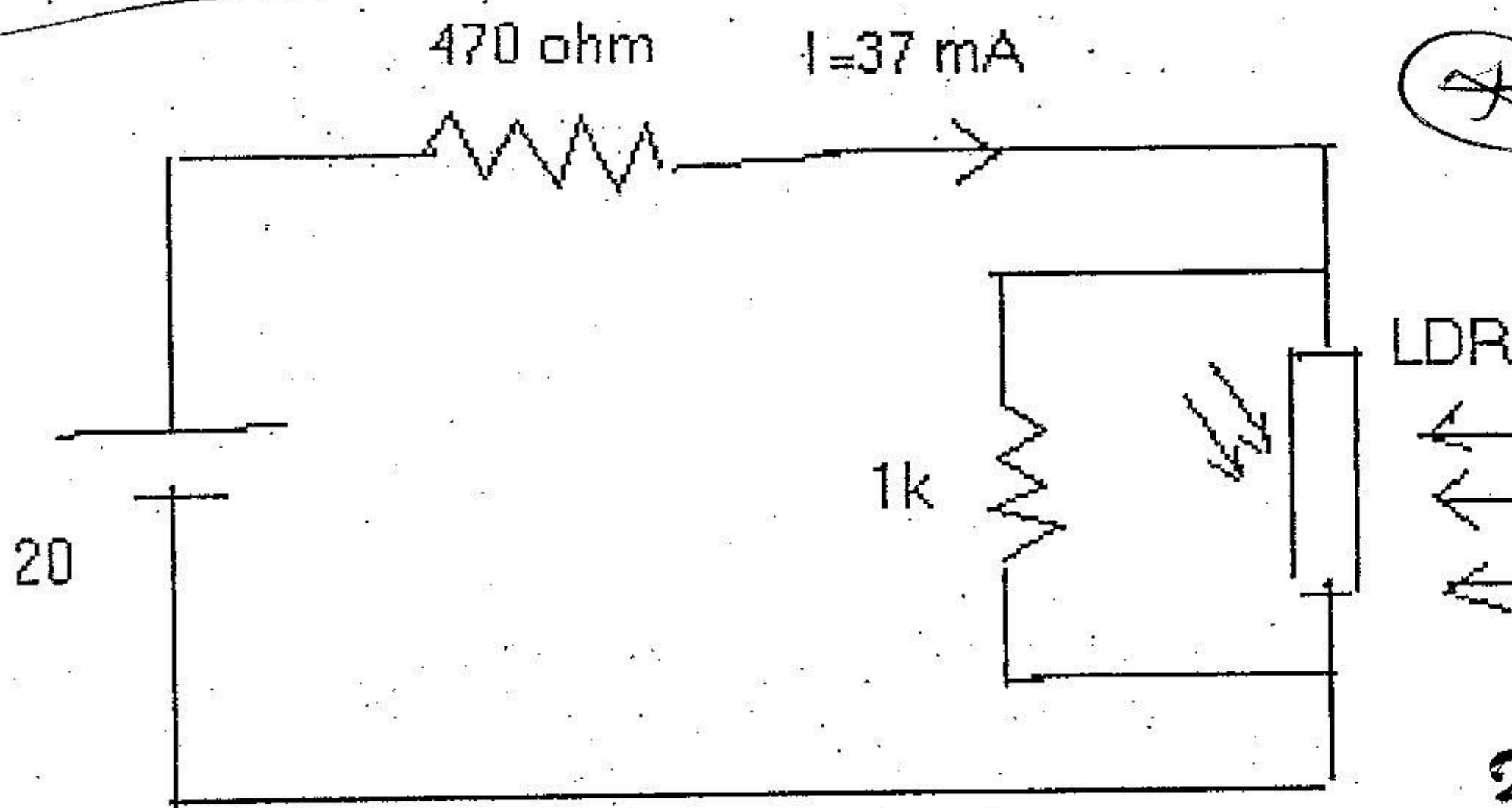$R_{LDRM} = 1k\Omega$
$V_{max} = 20 \text{ V}$
$V_{min} = 10 \text{ V}$



$$R_{eq} = 470 + (1 \parallel R_{LDR})$$

$$R_{eq} = 470 + \frac{R_{LDR}}{1+R_{LDR}}$$

$$20 = 37 \times 10^{-3} \left( 470 + \frac{R_{LDR}}{1+R_{LDR}} \right)$$


$$\frac{20}{37} \times 10^3 = 0.470 + \frac{R_{LDR}}{1+R_{LDR}}$$

$$\Rightarrow 540.5 = 0.470 + \frac{R_{LDR}}{1+R_{LDR}}$$

$$540.5 = \frac{R_{LDR}}{1+R_{LDR}} \Rightarrow 540.5 (1+R_{LDR}) = R_{LDR}$$

$$540.5 + 540.5 R_{LDR} = R_{LDR} \Rightarrow 540.5 = -539.5 R_{LDR} \Rightarrow R_{LDR} = \frac{540.5}{-539.5}$$

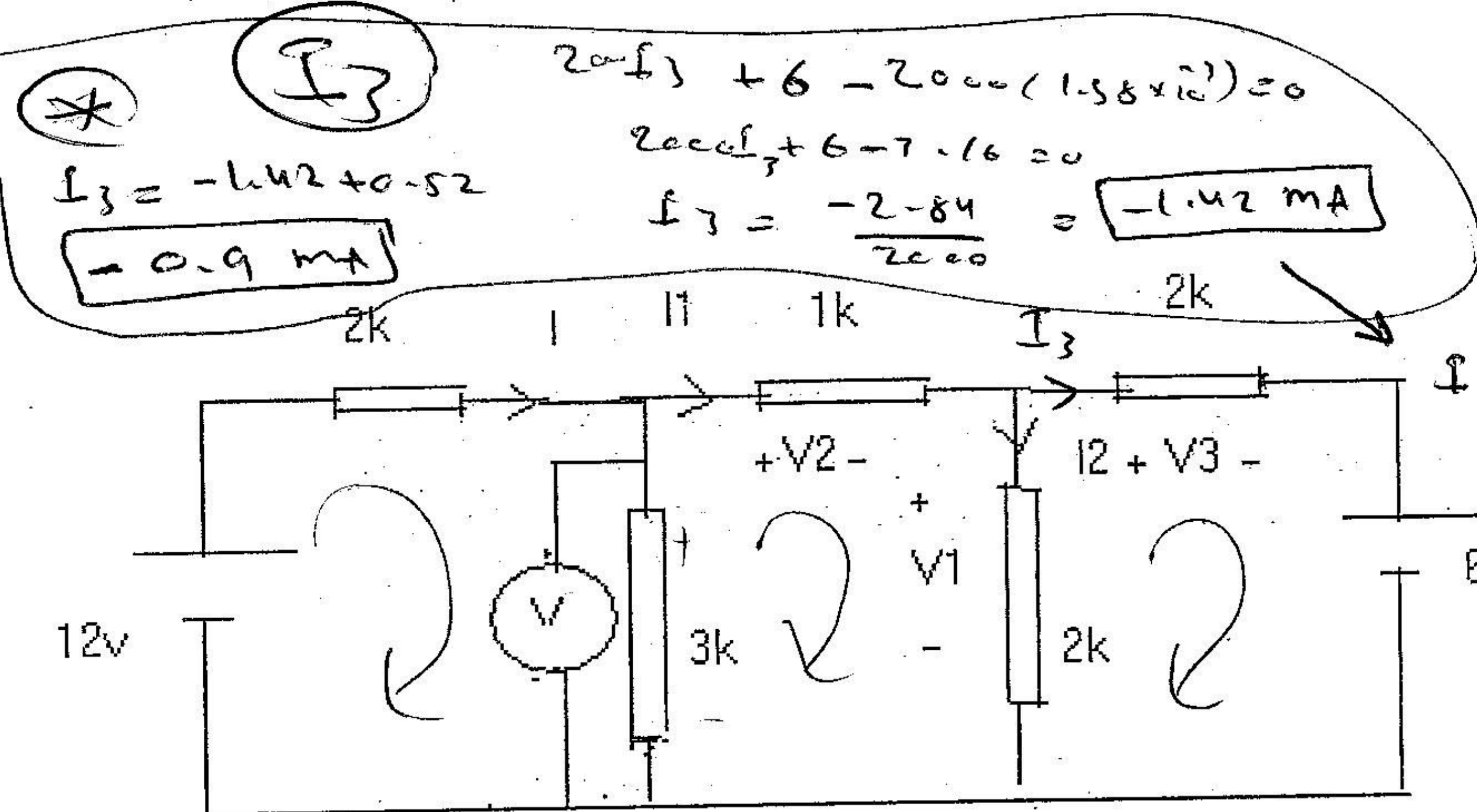Q5) For the circuit shown below if the voltmeter reading is 5 Volts. Find  $I, I_1, I_2, V_1, V_2, V_3$



$I_1 = 1.84 \text{ mA}$
$I_2 = 1.58 \text{ mA}$
$I = 3.5 \text{ mA}$
$V_1 = 3.16 \text{ V}$
$V_2 = 1.84 \text{ V}$
$V_3 = -1.8 \text{ V}$

$$V = 5 \text{ Volts} \Rightarrow V = IR \Rightarrow 5 = I(3000) \Rightarrow I = \frac{5}{3000} = 1.66 \text{ mA}$$

Loop 1:  $-12 + 2I + 3000(1.6 \times 10^{-3}) = 0 \Rightarrow -12 + 2000I + 5 = 0 \Rightarrow 2000I = 7 \Rightarrow I = \frac{7}{2000} = 3.5 \text{ mA}$

Loop 2:  $-5 + 1000I_1 + 2000I_2 = 0$

$$I_1 = 3.5 - 1.66 = 1.84 \text{ mA}$$

$$-5 + 1000(1.84 \times 10^{-3}) + 2000I_2 = 0 \Rightarrow -5 + 1.84 + 2000I_2 = 0$$

$$2000I_2 = 3.16 \Rightarrow I_2 = \frac{3.16}{2000}$$


$$I_2 = 1.58 \text{ mA}$$

$$V_1 = I_2(2000) = 1.58 \times 10^{-3} \times 2 \times 10^3 = 3.16 \text{ V}$$

$$V_2 = I_1(1000) = 1.84 \times 10^{-3} \times 1 \times 10^3 = 1.84 \text{ V}$$
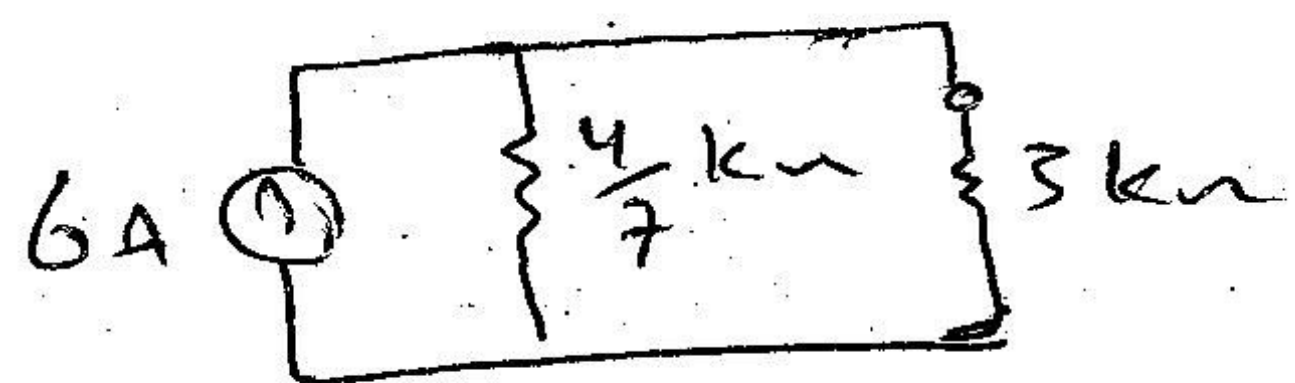
$$V_3 = I_3(2000) = 0.9 \times 10^{-3} \times 2 \times 10^3 = -1.8 \text{ V}$$







Norton Equivalent

Q6) For the circuit shown below, using Norton theorem find the power of  $3k\Omega$  resistor

$I_N =$	$6 \text{ mA}$
$V_{OC} =$	$9 \text{ V}$
$R_{TH} =$	$\frac{4}{7} \text{ k}\Omega$
$P_{3K} =$	$2.7 \text{ mW}$

$P_{3K} = \frac{I^2 R}{2}$   
 $I_{3K} = 6 \left( \frac{\frac{4}{7}}{\frac{4}{7} + 3} \right) = 0.95 \text{ mA}$

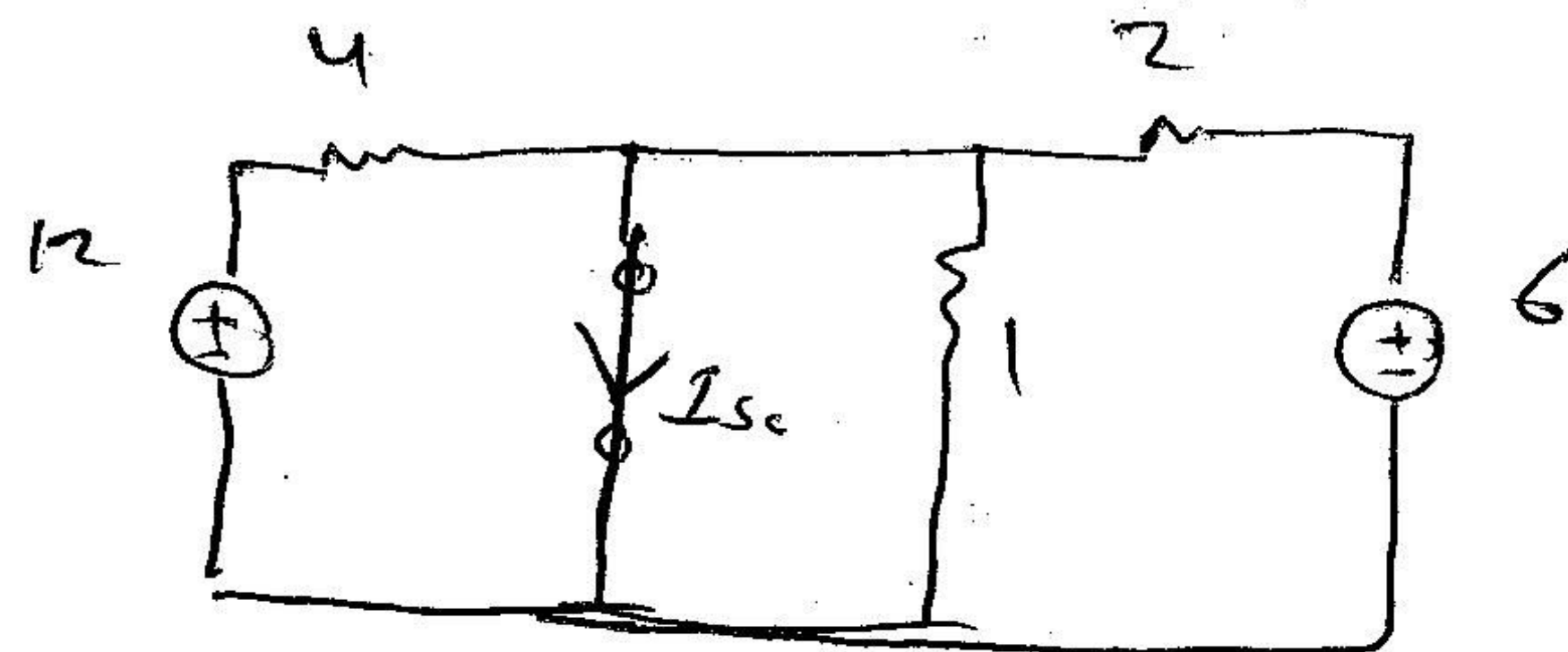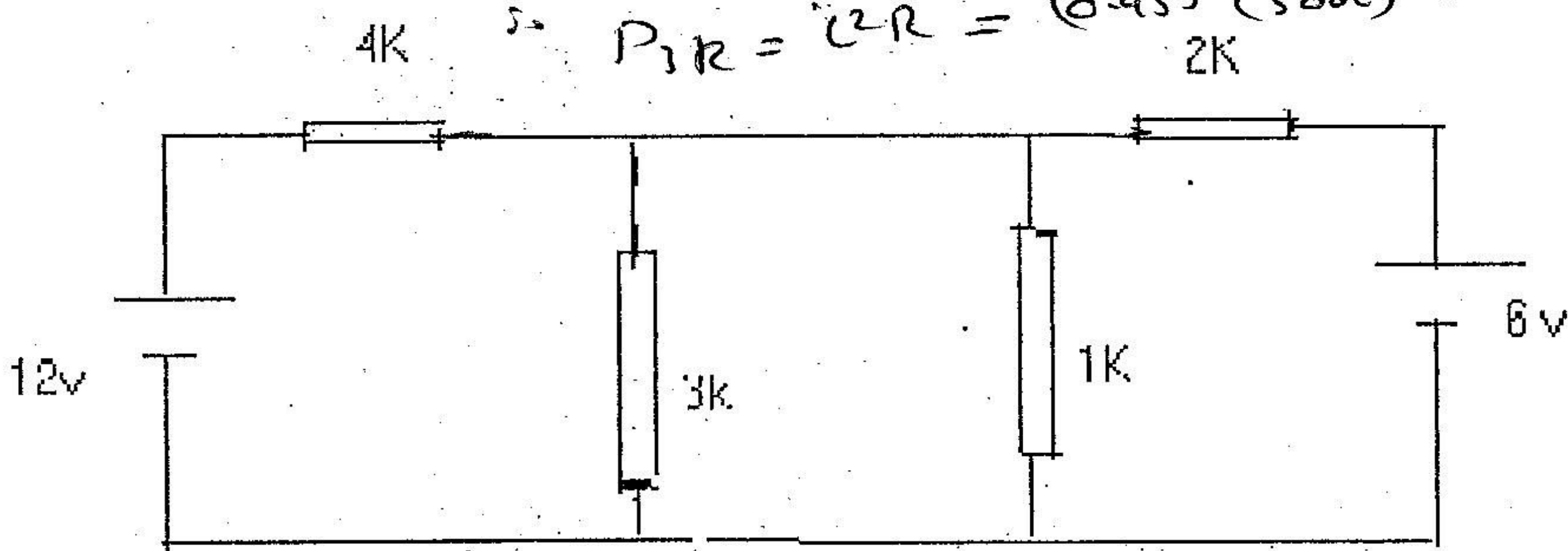$P_{3K} = I^2 R = (0.95)^2 (3000) = 0.9 \times 10^{-6} \times 3 \times 10^3 = 2.7 \times 10^{-3} = 2.7 \text{ mW}$



From using super position  $\Rightarrow$  from  $12 \text{ V}$   $\Rightarrow I_{sc1} = \frac{12}{4} = 3 \text{ mA}$

from  $6 \text{ V} \Rightarrow I_{sc2} = \frac{6}{2} = 3 \text{ mA}$

$\Rightarrow I_{sc} = 3 + 3 = 6 \text{ mA} = I_N$

$R_N \Rightarrow R_{eq} \leftarrow 4 \parallel 1 \parallel 2 \Rightarrow (1 \parallel 2) \parallel 4 \Rightarrow \frac{1 \times 2}{1+2} = \frac{2}{3}$   
 $\frac{2}{3} \parallel 4 = \frac{\frac{2}{3} \times 4}{\frac{2}{3} + 4} = \frac{\frac{8}{3}}{\frac{14}{3}} = \frac{8}{14} = \frac{4}{7} \text{ k}\Omega$

$V_{oc1} (\text{from } 12 \text{ V}) = 12 \text{ V} \quad V_{oc2} (\text{from } 6 \text{ V}) = 6 \left( \frac{1}{1+2} \right) = 3 \text{ V}$

Q7) Use superposition to find  $I$  in the circuit below

$\Rightarrow V_{oc} = 12 - 3 = 9 \text{ V}$

$I'$  from  $12 \text{ V}$  source


$I''$  from  $6 \text{ V}$  source

$I' = \frac{12}{1 \times 10^3} = 12 \text{ mA} = -12 \text{ mA}$

$I'' = \frac{6}{(2 \parallel 1)} = \frac{6}{\frac{2}{3}} = \frac{18}{2} = 9 \text{ mA}$

$I' =$	$-12 \text{ mA}$
$I'' =$	$9 \text{ mA}$
$I =$	$-3 \text{ mA}$

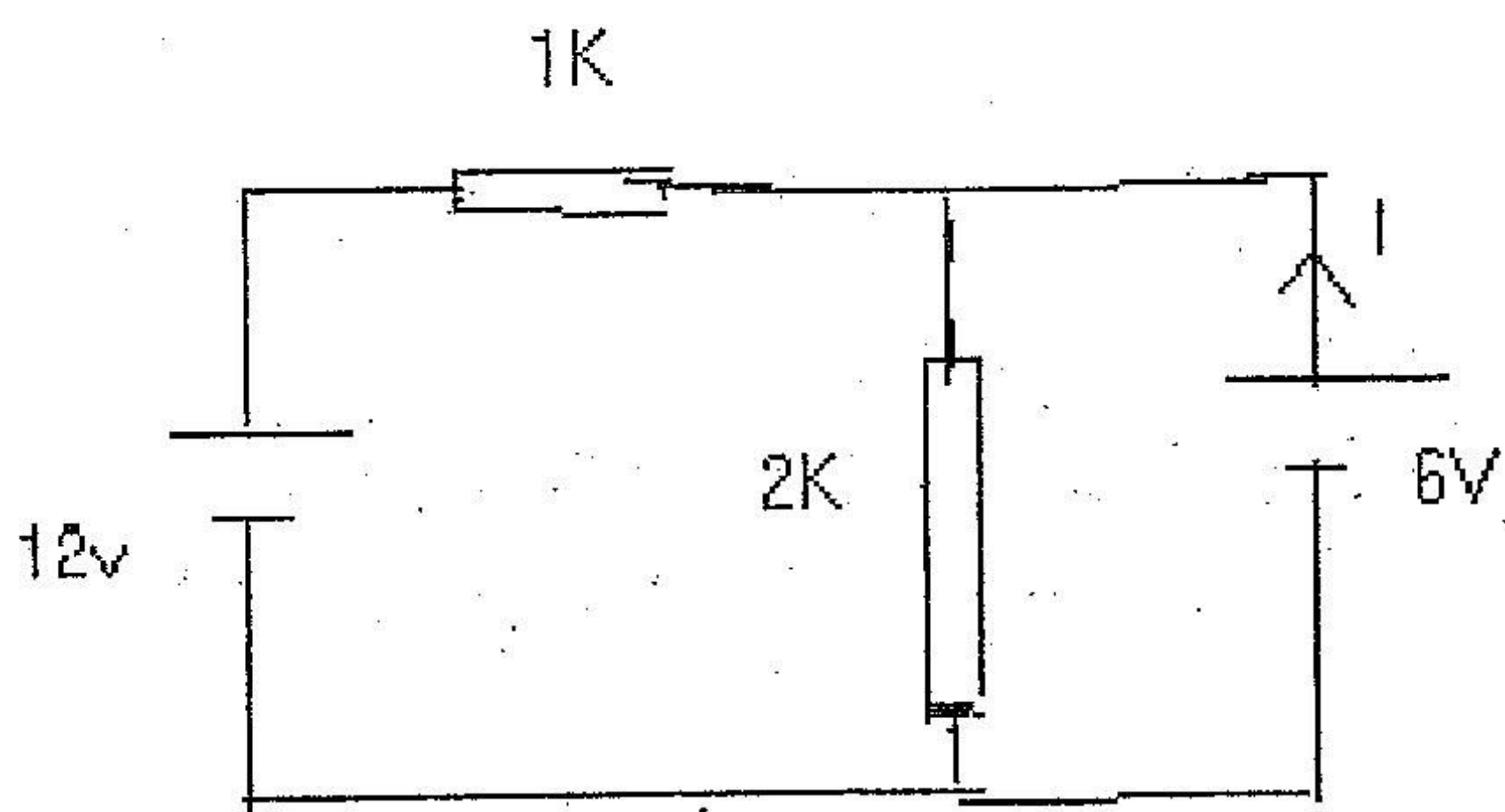$\rightarrow$  or by KVL  
 $12 \text{ V} \text{ w } -5 \text{ V}$



$\therefore I' + I'' = -12 + 9 = -3 \text{ mA}$